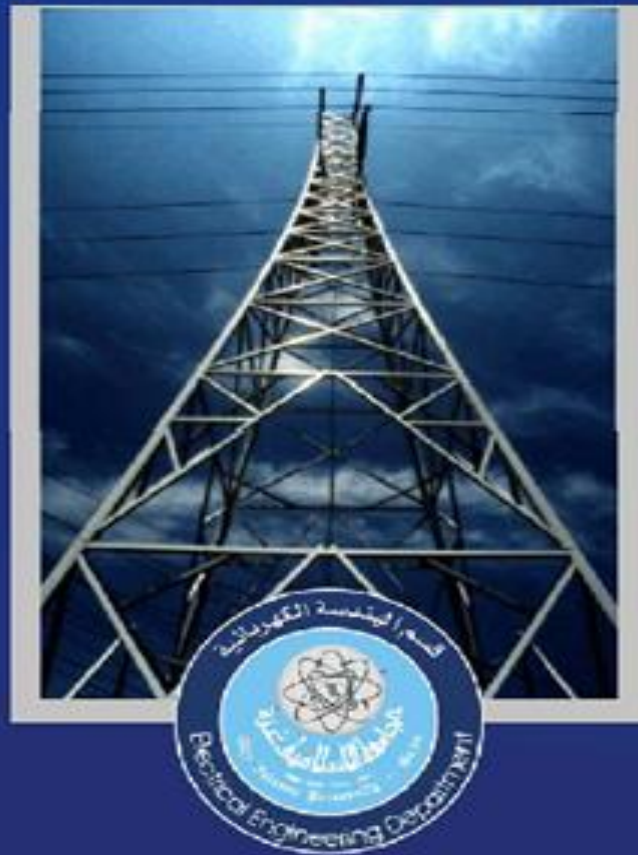


THE ISLAMIC UNIVERSITY OF GAZA



ELECTRICAL DEPARTMENT

Engineering Faculty

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

Islamic university –Gaza

Electrical Engineering

Electronic II Lab



Experiment: 1

Multistage Amplifier: Part I



Eng.Mohammed Elasmer

• **Application of BJT:**

(1) Amplification (linear mode)

(2) Switching (cutoff-saturation region)

(3) Isolation


(isolate small current circuit from large current circuit)

•Steps of Amplification:

(1) Biasing (applying DC voltage)

- To activate Transistor
- To get Linear mode

(2) Applying input AC signal

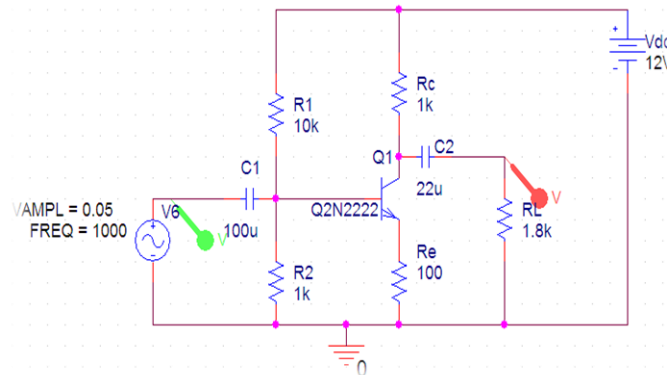

Multistage Amplifier



```
graph TD; A[Multistage Amplifier] --> B[One Stage BJT Amplifier]; A --> C[Two Stage BJT Amplifier]; B --> D[No load State]; B --> E[1.8k load]; C --> F[No load state]; C --> G[1.8K load];
```

One Stage BJT Amplifier

No load State

1.8k load

Two Stage BJT Amplifier

**No load
state**


1.8K load

Two port system


$$A_{vnl} = \frac{V_o}{V_i}$$

$$V_o = V_i * A_{vnl} = E_{th}$$

$$V_i = I_i * Z_{in}$$

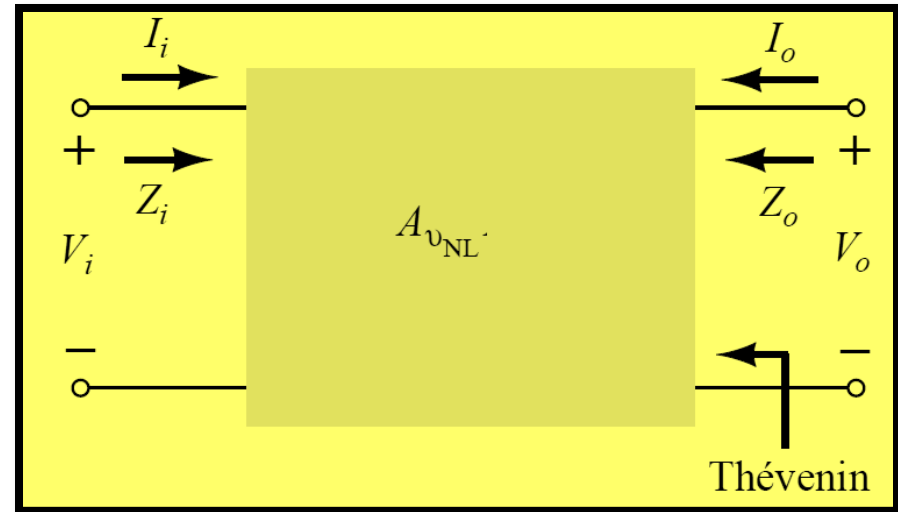


□ No Load State

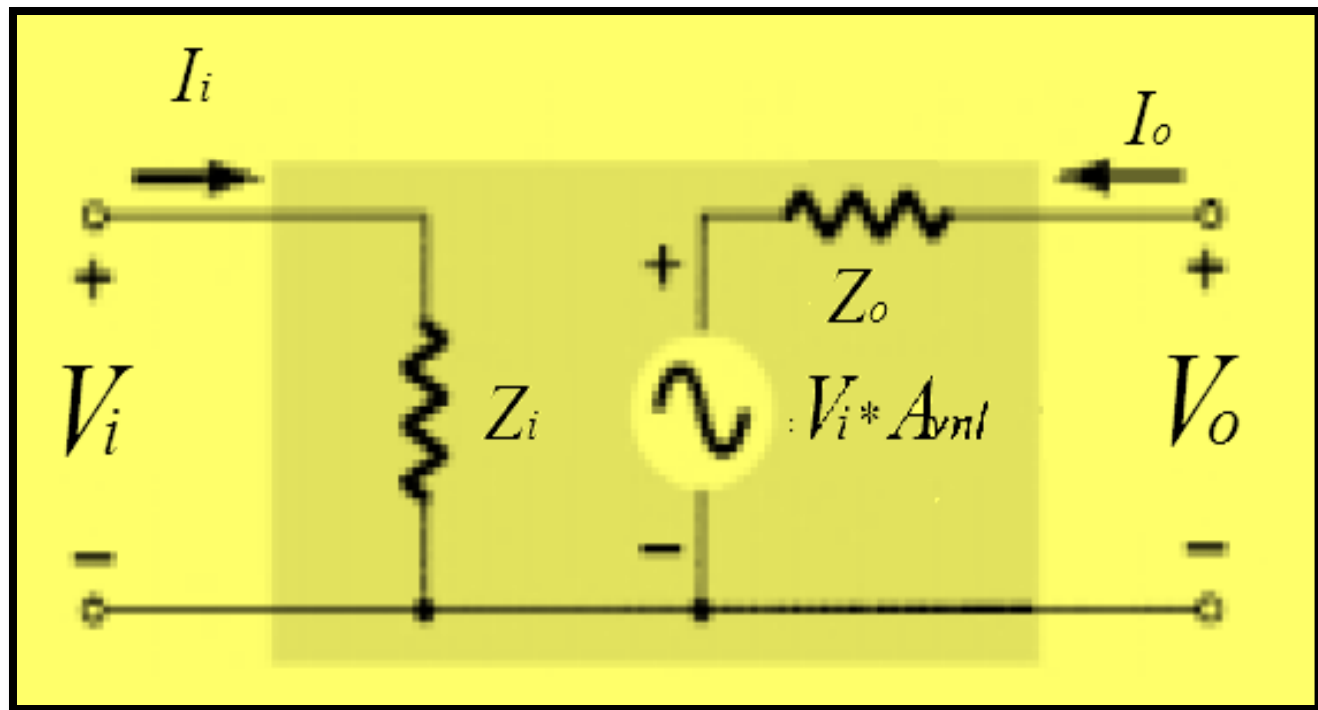

$$V_o = V_i * A_{vnl}$$

$$V_i = I_i * Z_{in}$$

□ With RL Load

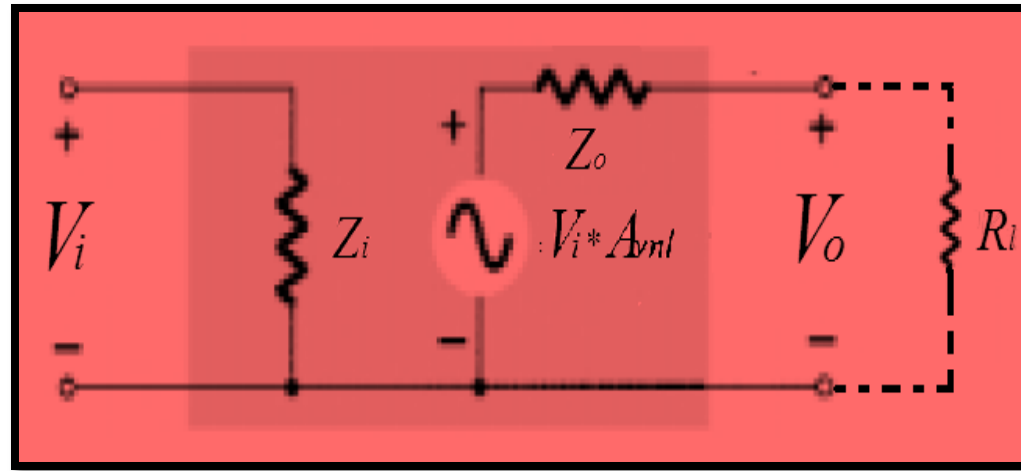

$$V_o|_{\text{voltage divider}} = \frac{R_l}{R_l + Z_o} * V_i \cdot A_{vnl}$$

$$\frac{V_o}{V_i} = \frac{R_l}{R_l + Z_o} * A_{vnl} = A_{vloaded}$$

$$A_{vloaded} = \frac{R_l}{R_l + Z_o} * A_{vnl}$$


Note :

$$*** A_{vnl} > A_{vloaded}$$

$$*** Z_o = R_c(\text{from re model})$$

Part One: One stage BJT Amplifier

No load state

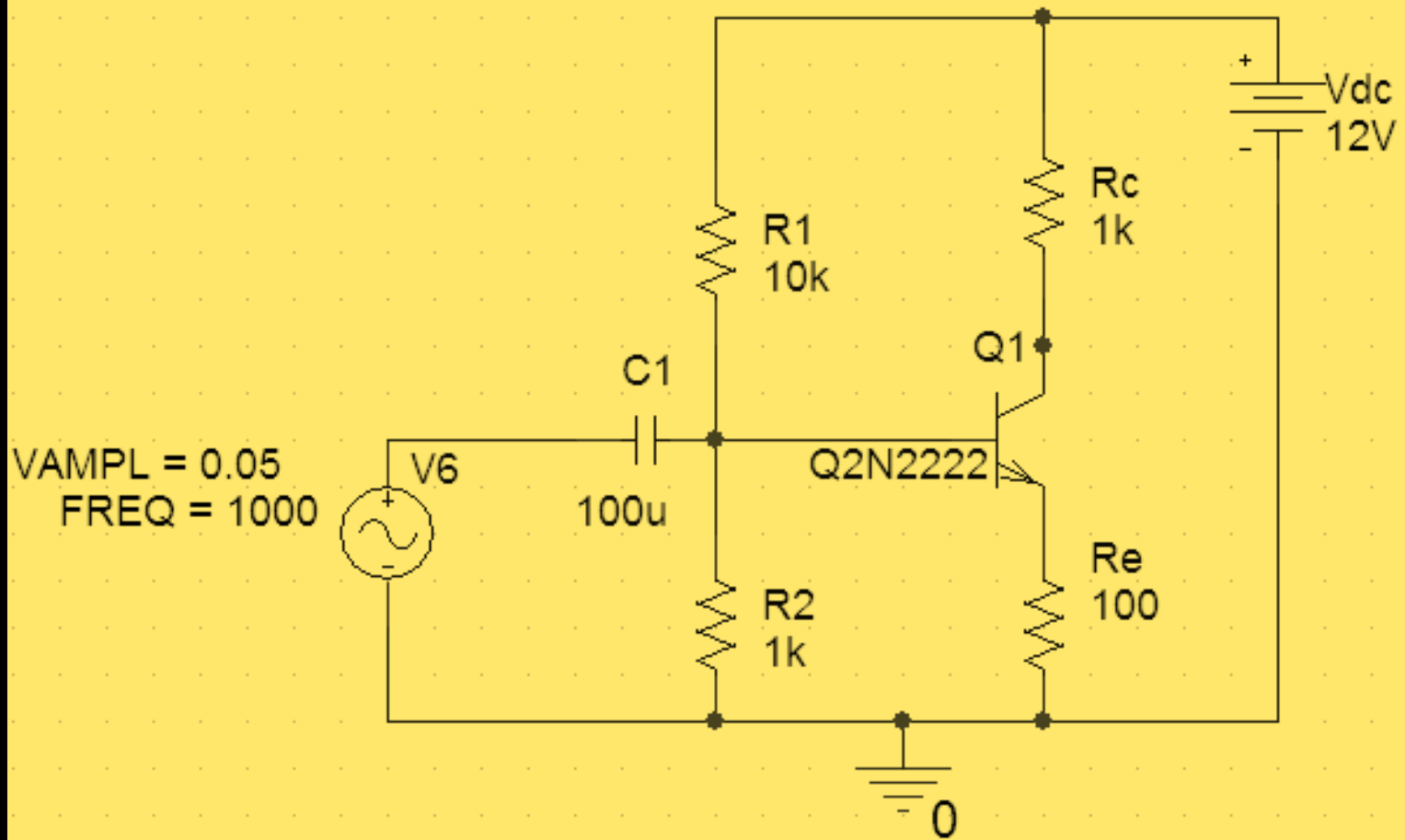

Results:

[1] Calculation:

From re model

$$A_{nl} = -\frac{R_c}{R_e} = -10$$

Results:

[2] Practical:

(A) Using Multimeter to measure V_i & V_o

$$A_{vnl} = \frac{V_o}{V_i} =$$

?

(B) Using Oscilloscope to display V_i & V_o


Results:


[3] Simulation (Orcad 9):

$$A_{vloaded} = \frac{R_l}{R_l + Z_o} * A_{vnl}$$

when R_L is very high $\sim 1000\text{k}\Omega$

then $A_{vloaded} = A_{vnl}$

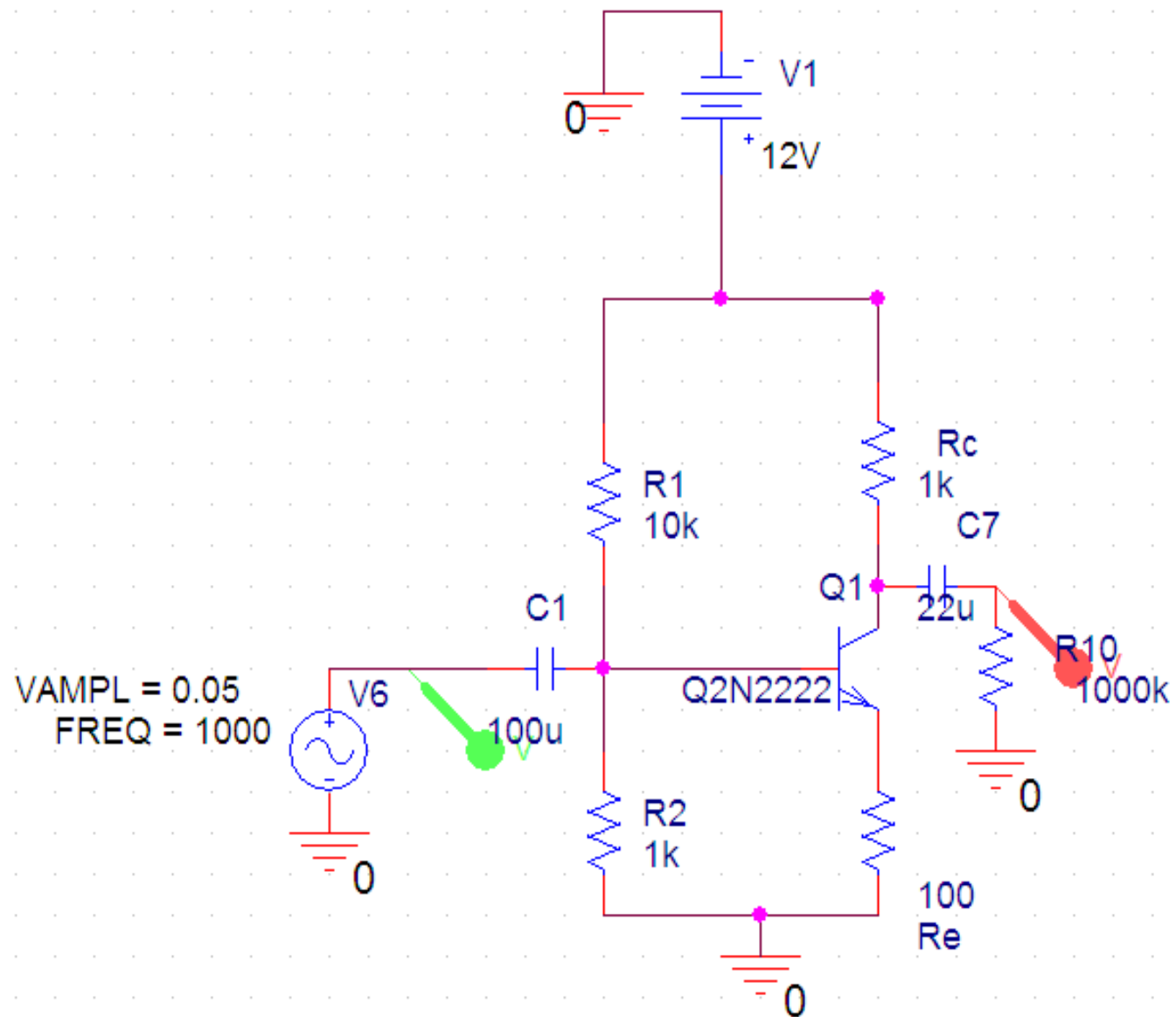


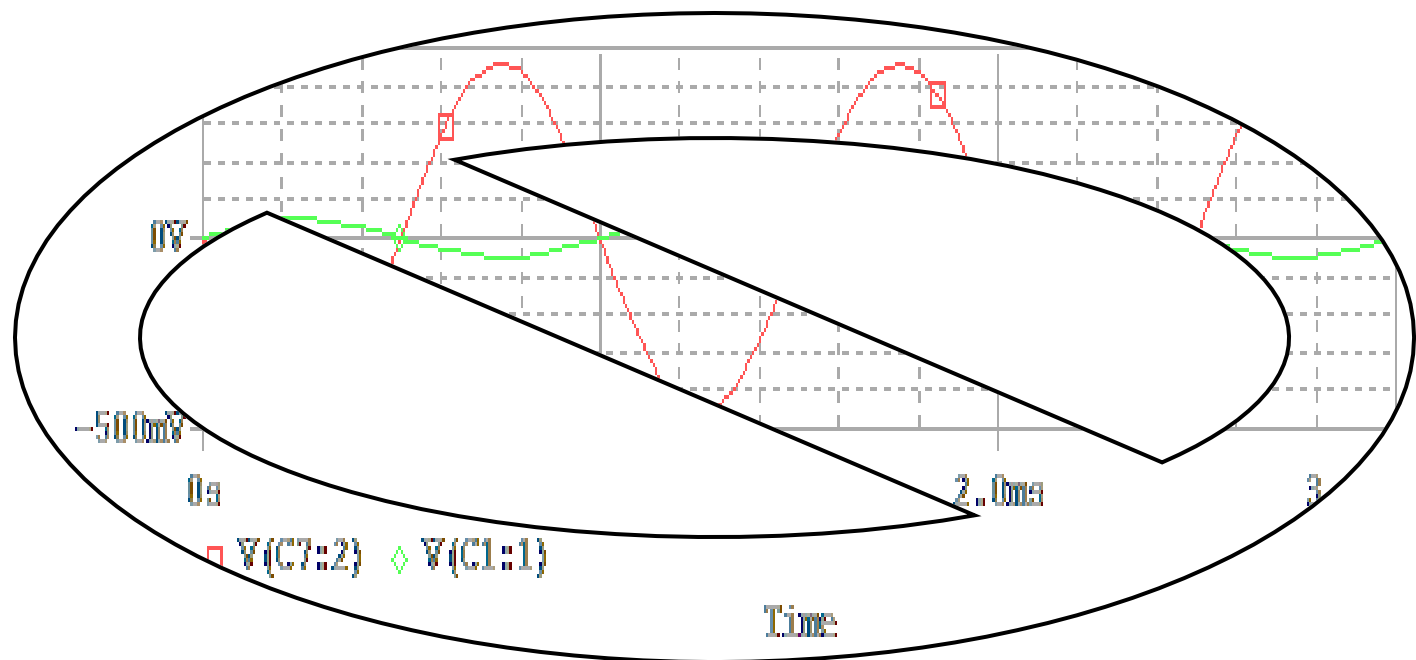

$$A_{vnl} = \frac{V_o}{V_i} =$$

?

With 1.8k load

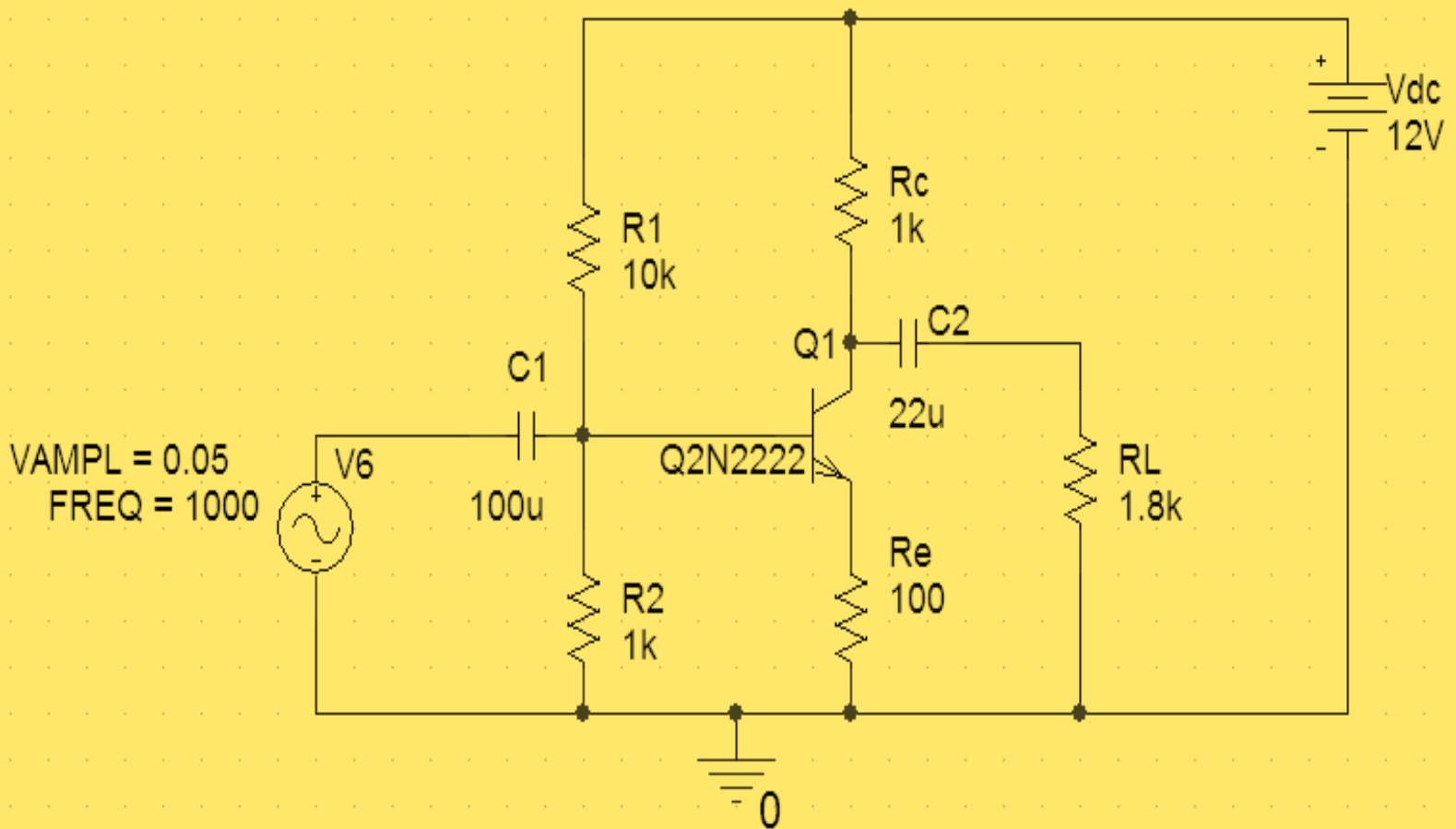

Results:

[1] Calculation:

$$A_{nl} = -\frac{R_c}{R_e} = -10 \text{ (From re model)}$$

$$A_{vloaded} = \frac{R_l}{R_l + Z_o} * A_{vnl}$$

$$= \frac{1.8}{1.8 + 1} * 10 = 6.428 \quad , , , \text{ where } Z_o = R_c$$

Results:

[2] Practical:

(A) Using Multimeter to measure V_i & V_o


$$A_{loaded} = \frac{V_o}{V_i} =$$


?

(B) Using Oscilloscope to display V_i & V_o

Results:

[3] Simulation (Orcad 9):

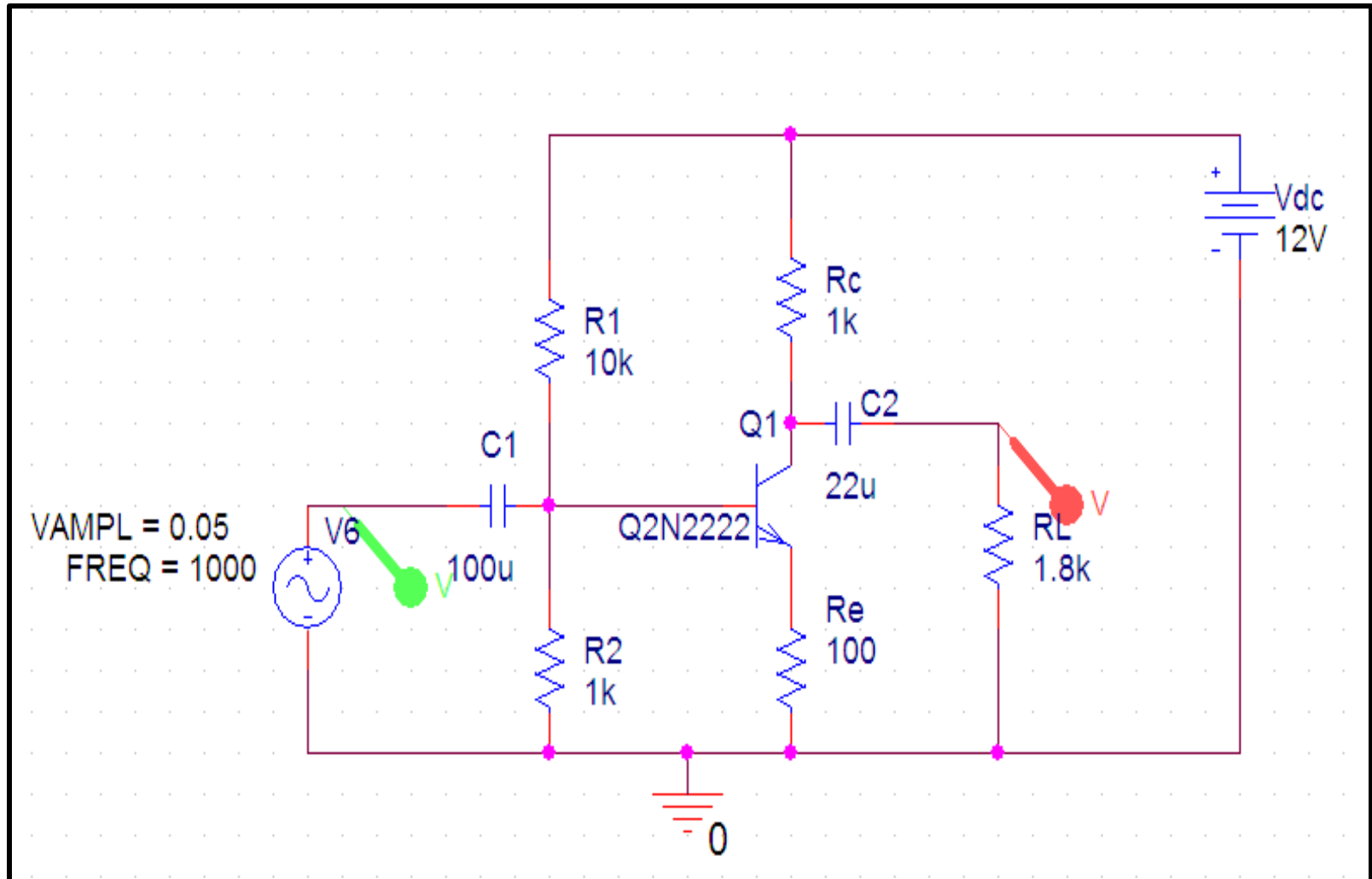

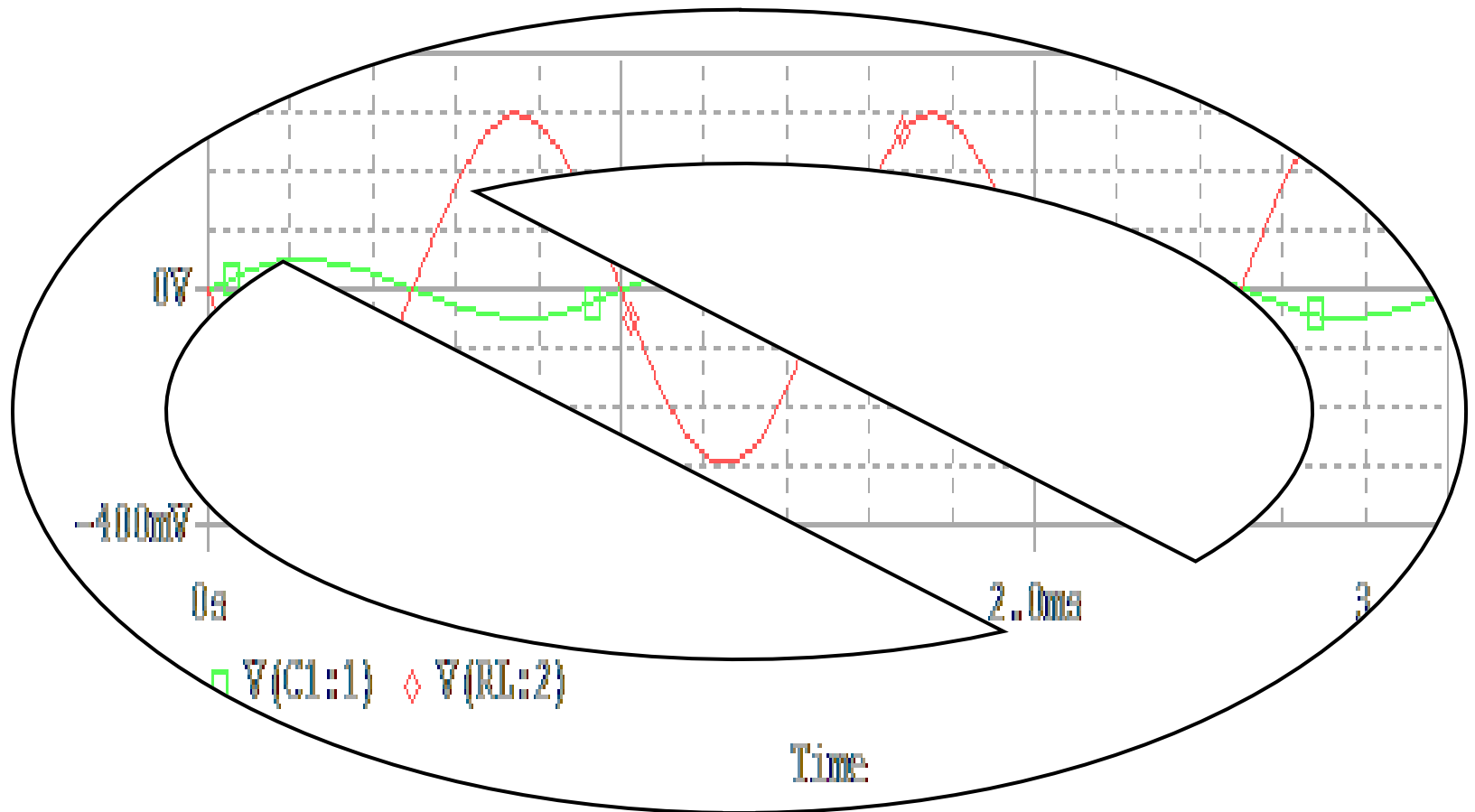


$$A_{loaded} = \frac{V_o}{V_i} =$$

?

Part Two

Two stage BJT Amplifier

Part Two: Two stage BJT Amplifier

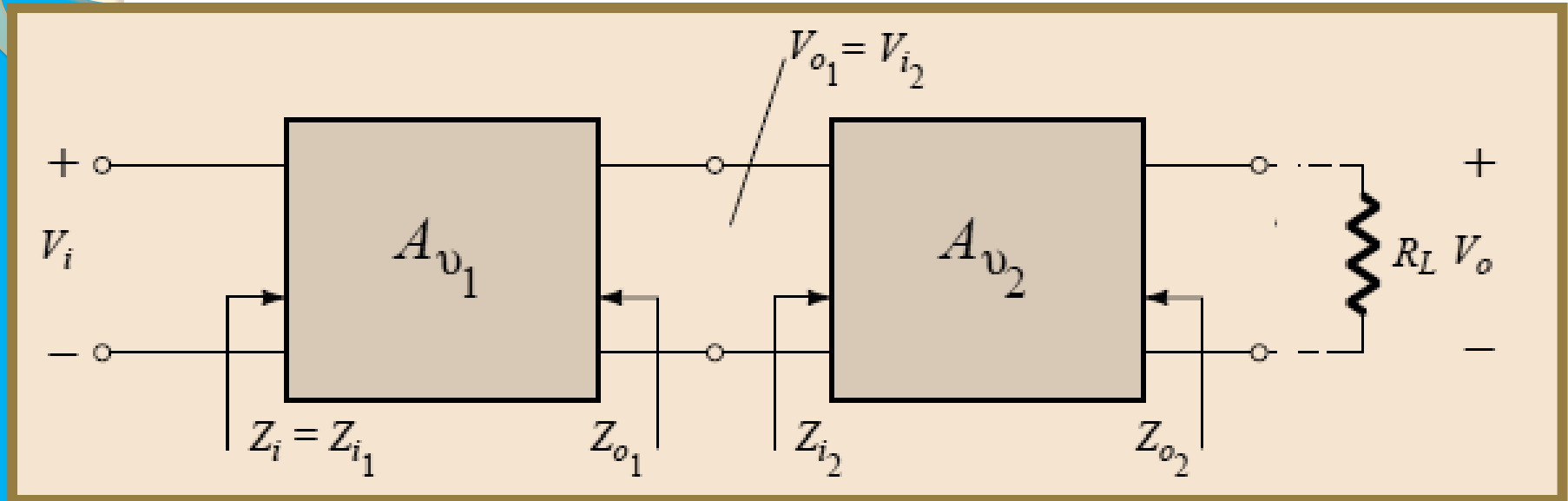

Cascade connection :

In which each stage is coupled with the next by a capacitor.

(I) With no load


[1] Calculation:

$$\begin{aligned} A_{vnl(tot)} &= A_{vloaded(1)} * A_{vnl(2)} \\ &= \left(\frac{Z_{in2}}{Z_{in2} + Z_{o1}} A_{vnl(1)} \right) * A_{vnl(2)} \end{aligned}$$

$$Z_{o1} = R_c = 1 \text{ k}\Omega$$

$$Z_{i2} = RB1 // RB2 // \beta(re + R_e) = \sim 0.8 \text{ k}\Omega$$
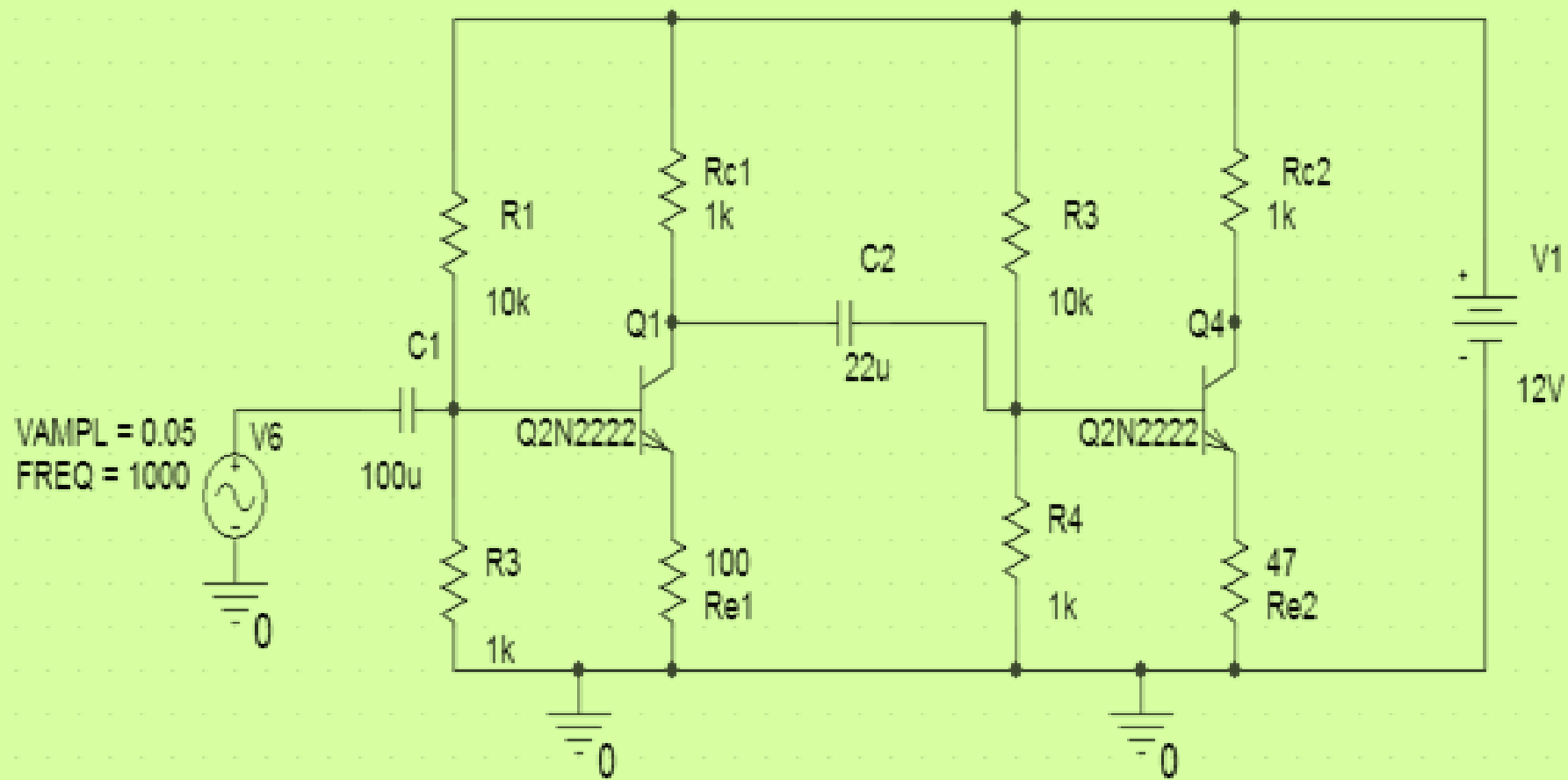
$$\begin{aligned} A_{vnl(tot)} &= \left(\frac{0.8}{0.8+1} A_{vnl(1)} \right) * A_{vnl(2)} \\ &= 0.44 * 10 * 21.276 = 94.56 \end{aligned}$$



Results:

[2] Practical:

(A) Using Multimeter to measure V_i & V_o


$$A_{nl(tot)} = \frac{V_o}{V_i} =$$


?

(B) Using Oscilloscope to display V_i & V_o

Results:

[3] Simulation (Orcad 9):

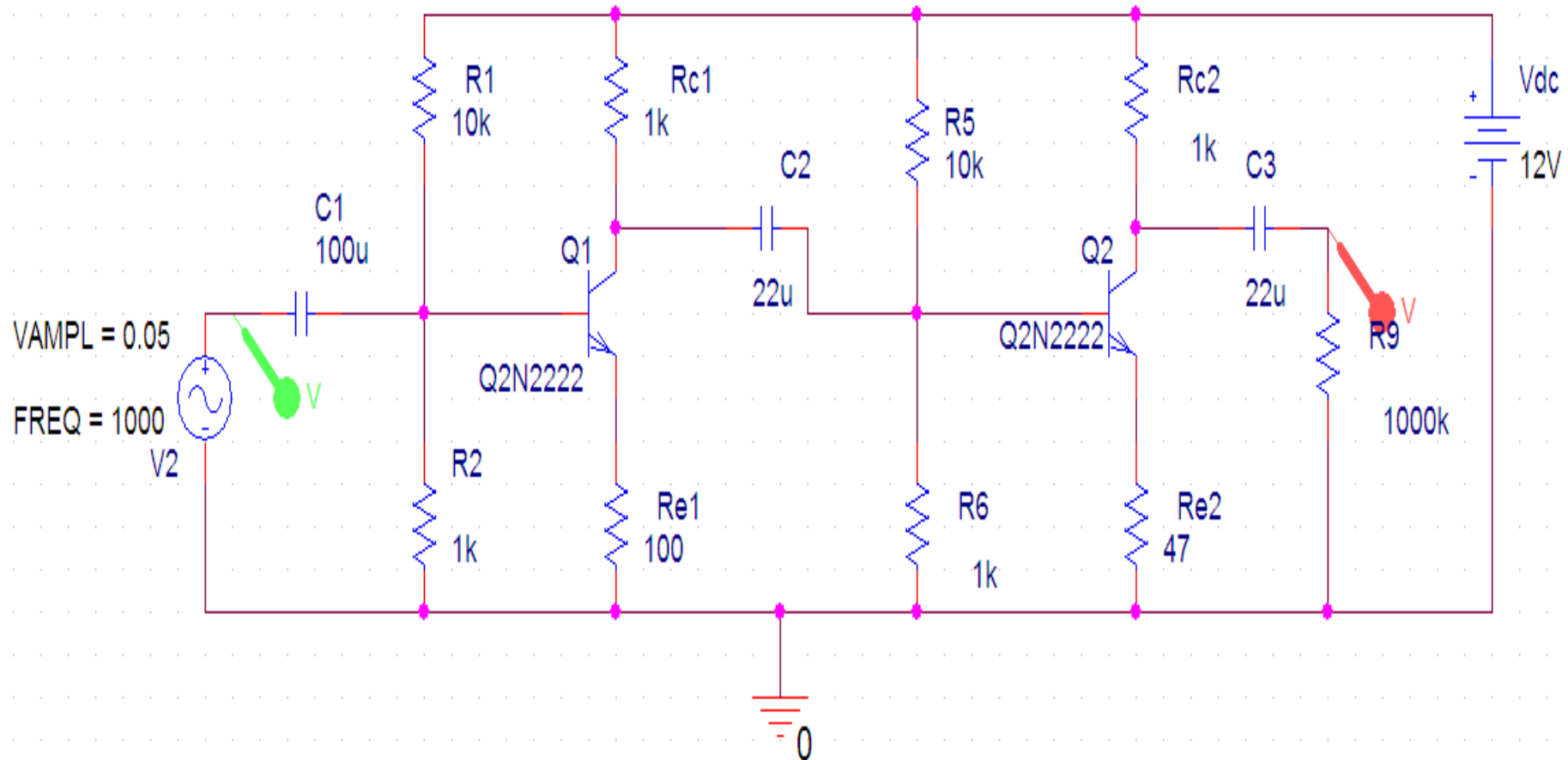

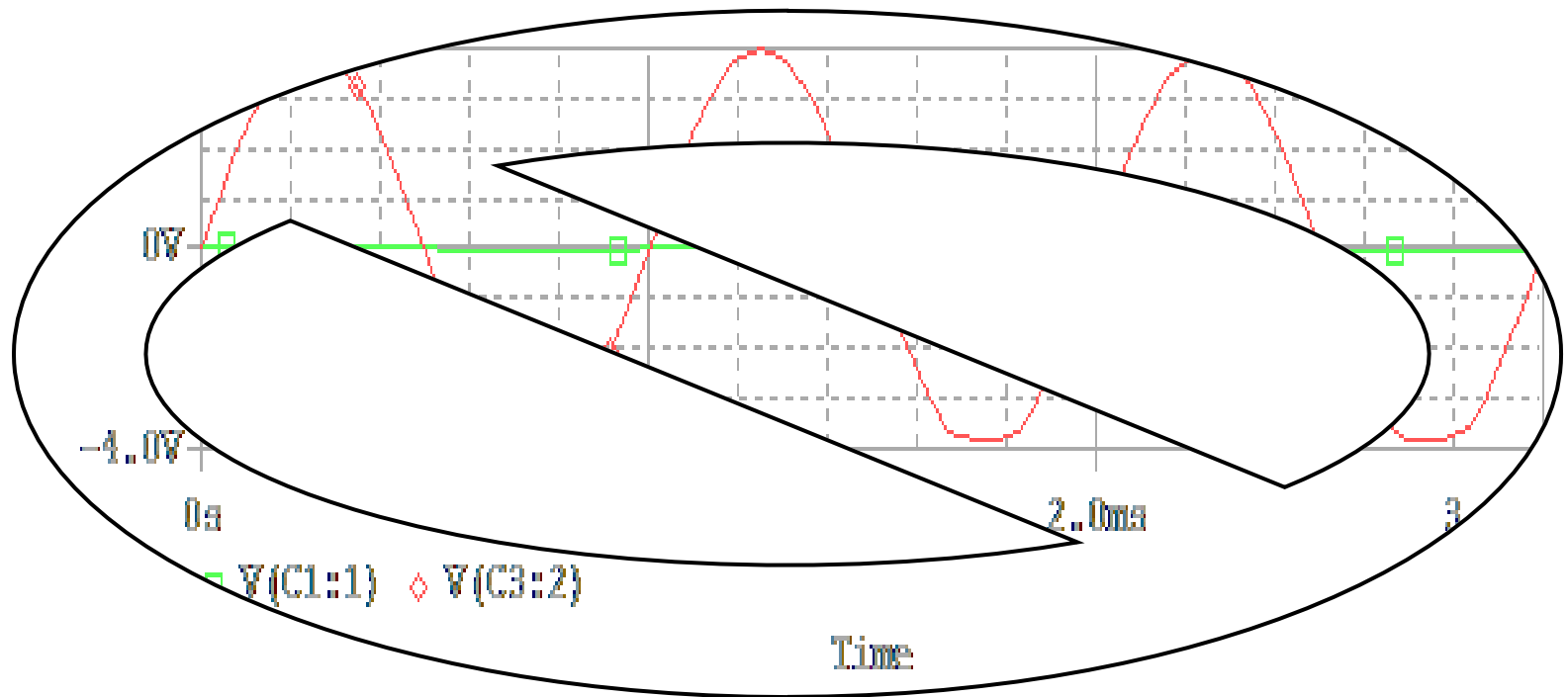

$$A_{vnl}(tot) = \frac{V_o}{V_i} =$$

?

(I) With 1.8k load

[1] Calculation:

$$\begin{aligned} A_{vloaded(tot)} &= A_{vloaded(1)} * A_{vloaded(2)} \\ &= \left(\frac{Z_{in2}}{Z_{in2} + Z_{o1}} A_{vnl(1)} \right) * \left(\frac{R_L}{R_L + Z_{o2}} A_{vnl(2)} \right) \\ &= \left(\frac{0.8}{0.8 + 1} * 10 \right) * \left(\frac{1.8}{1.8 + 1} * 21.276 \right) \\ &= 60.7 \end{aligned}$$

$$Z_{o1} = R_c = 1 \text{ k}\Omega$$

$$Z_{i2} = R_{B1} // R_{B2} // \beta(r_e + R_e) \approx 0.8 \text{ k}\Omega$$

Results:

[2] Practical:

(A) Using Multimeter to measure V_i & V_o


$$A_{loaded(tot)} = \frac{V_o}{V_i} =$$


?

(B) Using Oscilloscope to display V_i & V_o

Results:

[3] Simulation (Orcad 9):

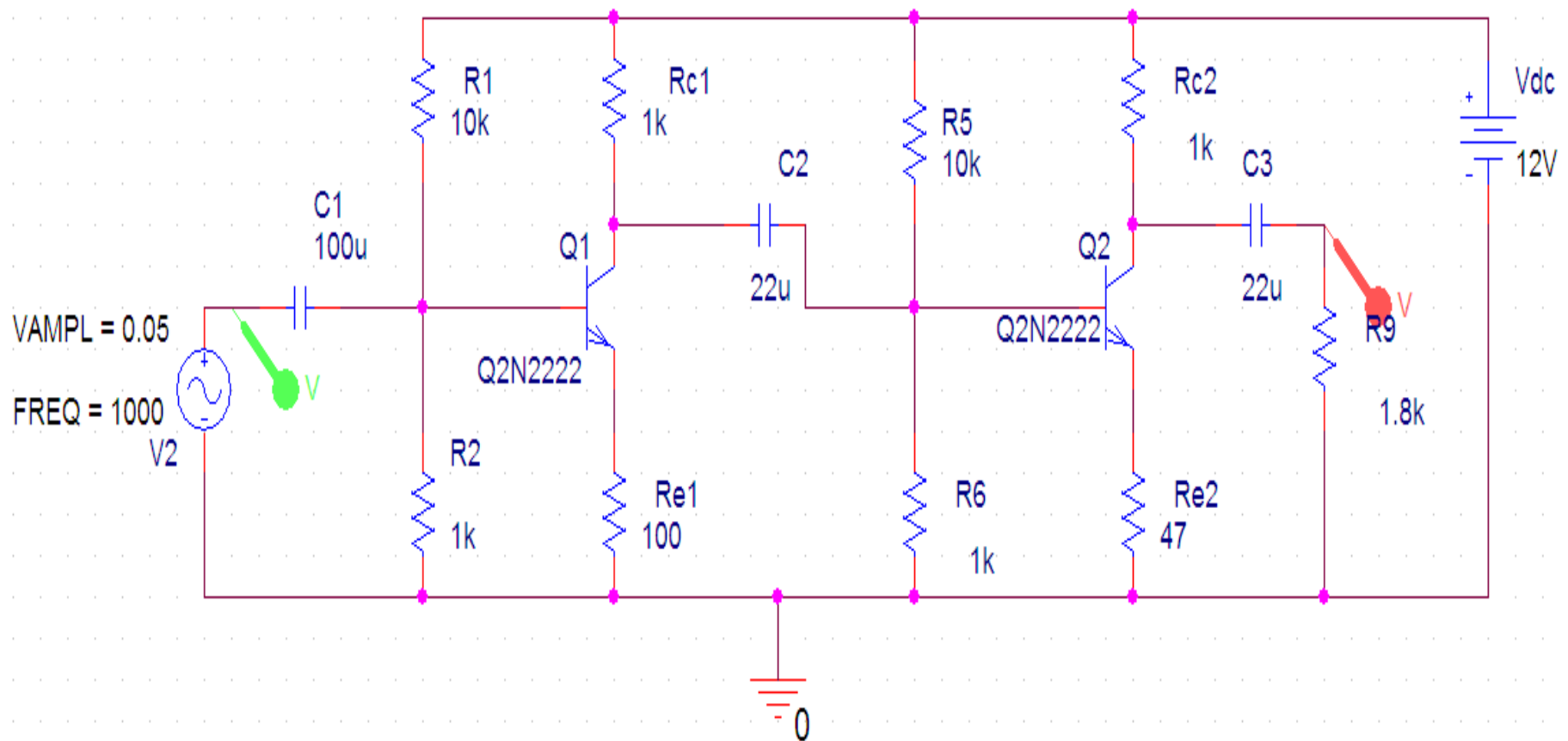

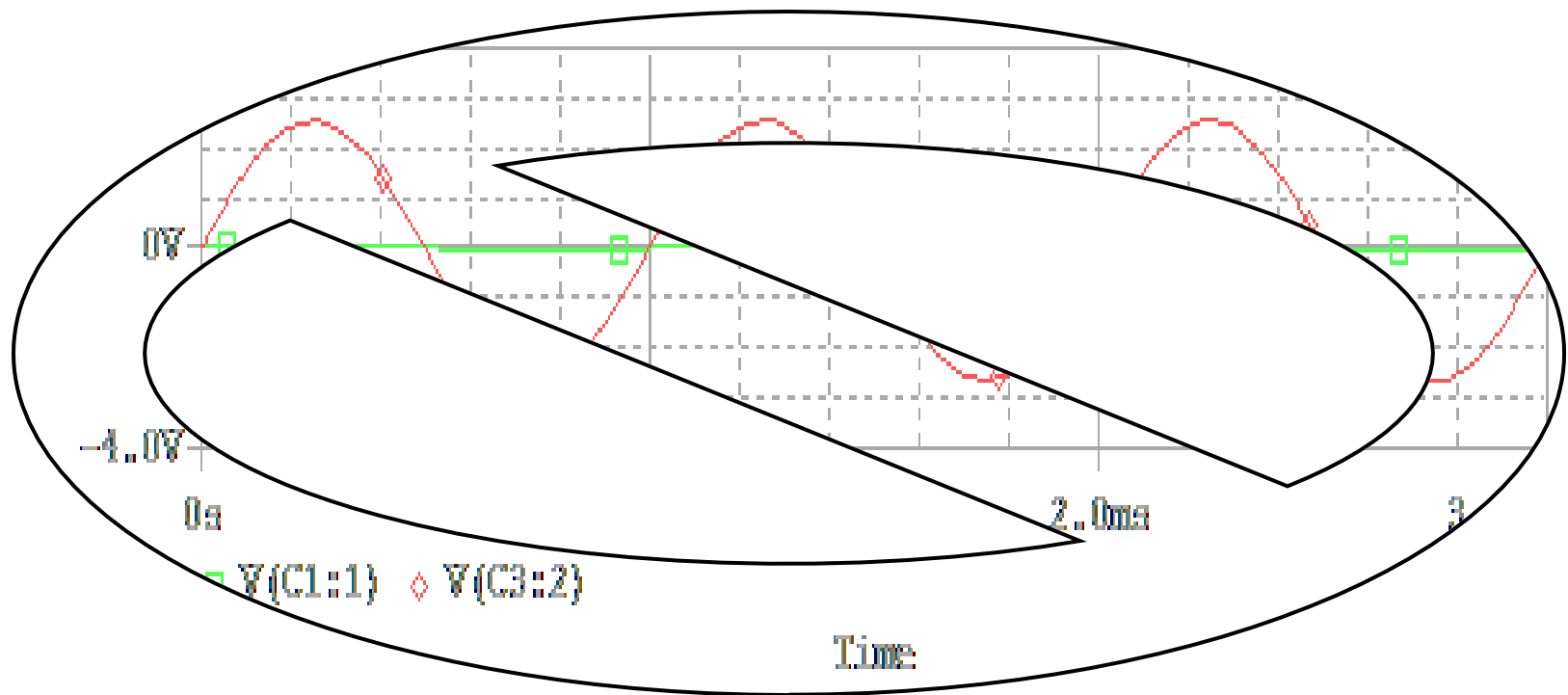

$$A_{loaded(tot)} = \frac{V_o}{V_i} =$$

?



Thank You !